

Example #13: A generator at City A delivers power at 1000 kW to City B. The total resistance in the cables is only 10 ohms.

- a) How much power is lost if delivered at: 5000 V; 500 000 V.
- b) Determine the efficiency rating for both voltages in a).

a) Find current drawn from source:

$$P = IV$$

$$\textcircled{1} 1000\,000 = I(5000)$$

$$I = 200\text{ A}$$

Now find power lost in lines:

$$P = I^2 R = 200^2 (10)$$

$$\boxed{P = 400\,000\text{ W}}$$

$$\textcircled{2} 1000\,000 = I(500\,000)$$

$$I = 2\text{ A}$$

$$P = I^2 R = 2^2 (10)$$

$$\boxed{P = 40\text{ W}}$$

$$\text{b) efficiency} = \frac{\text{useful power out}}{\text{power in}} \times 100$$

$$= \frac{1000\,000 - 400\,000}{1000\,000} \times 100 = \boxed{60\%}$$

$$\text{or} \\ = \frac{1000000 - 40}{1000\,000} \times 100 = \boxed{99.996\%}$$